

Design of 6T SRAM Array

Instructor : Dr Anuj Grover



INDRAPRASTHA INSTITUTE *of*
INFORMATION TECHNOLOGY
DELHI

Independent Project

Nikhil Pratap Singh MT21199
Sudhanshu Trivedi MT21212



Problem Statement:

$I_{cell} \geq 50\mu A$ at wc, 1.0V

$I_{leak} < 100pA$ at nom, 1.1V, 25C

$V_{min} = 0.95V$

Case-1: 6T Cell based BL=512 rows

Case-2: 6T Cell based BL=32 rows/ bank (16 banks)

Understanding:

$I_{cell} \geq 50\mu A$ at Worst case condition at 1V, 125C and $I_{leak} < 100pA$ at Nominal condition at 1.1V, 25C.

For calculating FOMs (Write margin, Write time, SNM, Retention Voltage) at $V_{min} = 0.95V$.


We have 2 cases with different total Bit line capacitance one with 512 rows and Second with 32 rows/bank with total such 16 banks

Various Conflicting Parameters -

For high cell current we need to increase the size of PG and PD but that leads to an increase in the leakage current too. We need to reach a sizing such that both the specifications can be met.

Verification Plan -


We tried different V_t devices with the width constraint and low voltage but were unable to achieve it. So, cell current specification was met at PVT of TT/25/1.08v with Standard Voltage devices.



Design Schematic(s)




Cell Ratio (CR)	1.46
Pull up ratio (PR)	0.7
W/L of PU	0.135/0.065
W/L of PD	0.255/0.065
W/L of PG	0.175/0.065

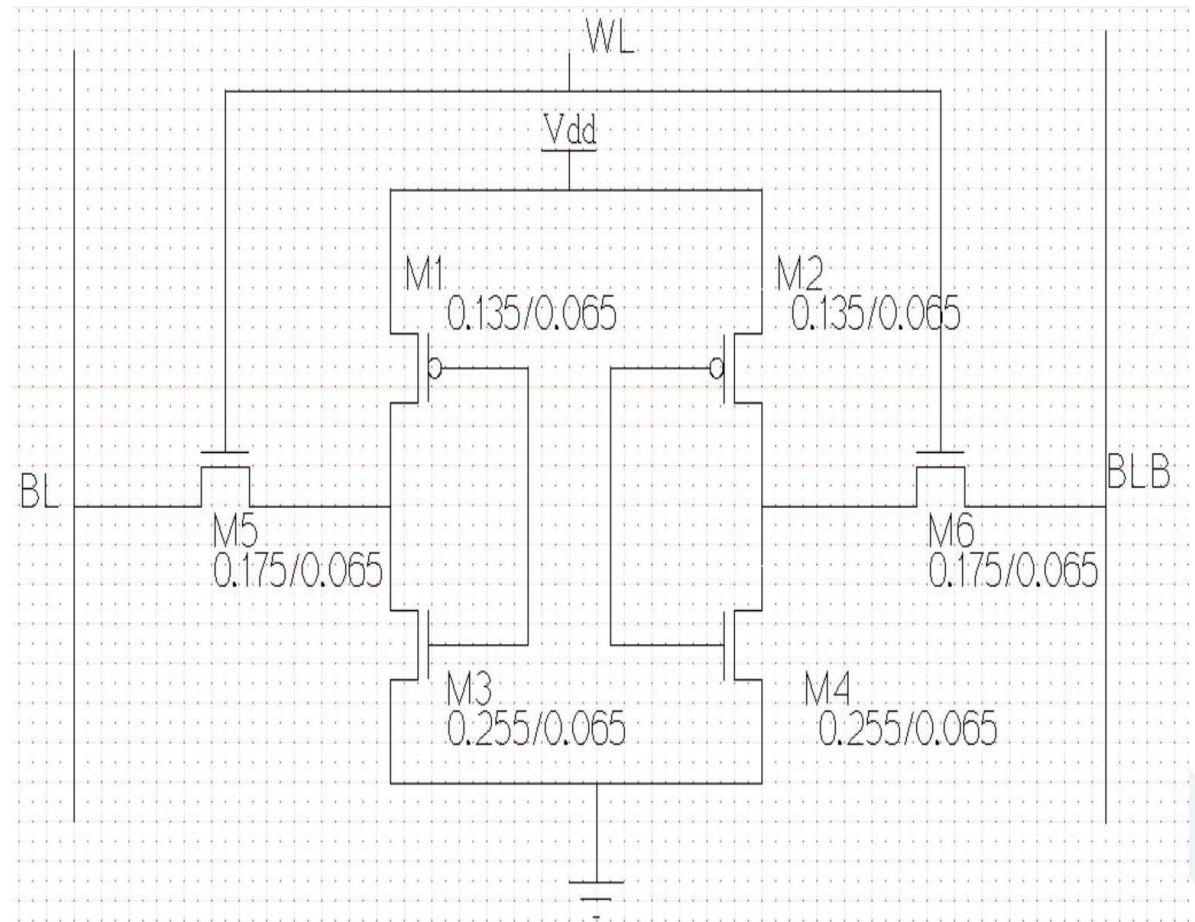



6T SRAM Cell Layout




AREA = $1.7\mu\text{m}^2$

 

DRC/LVS clean

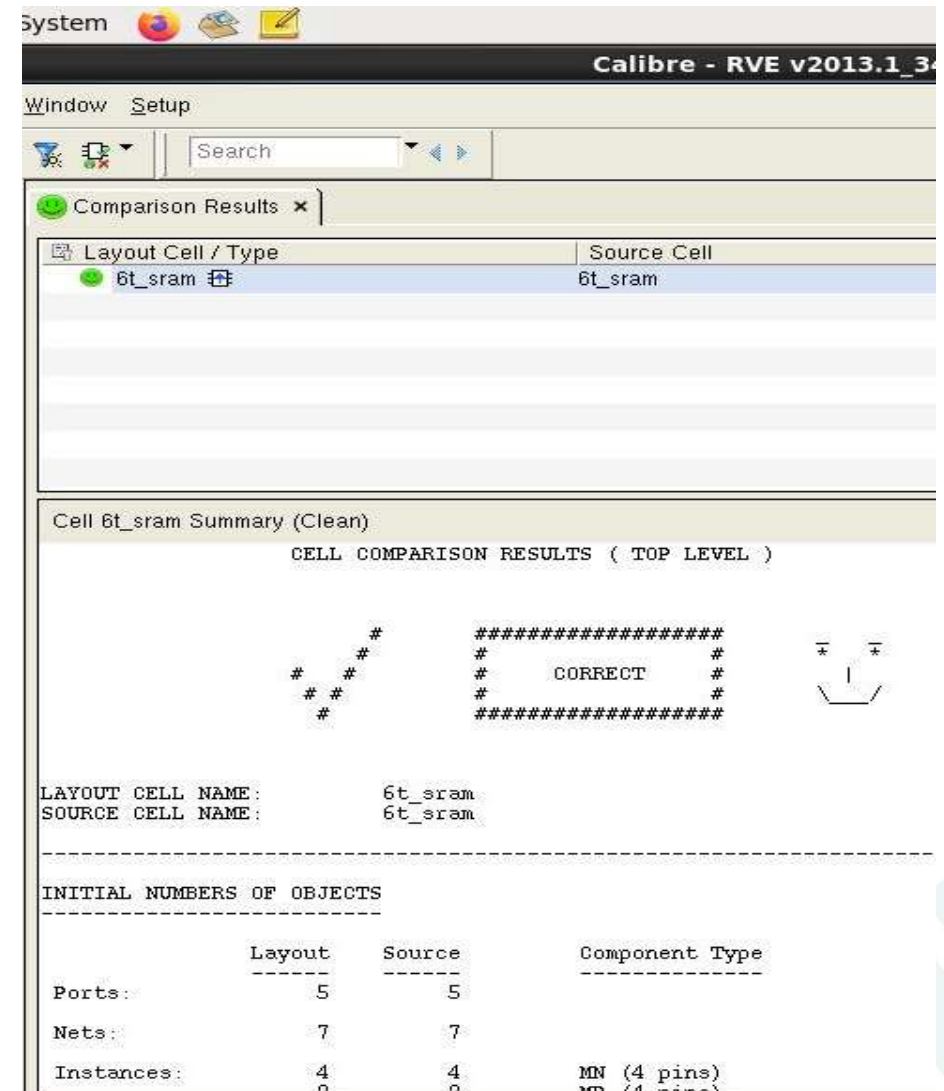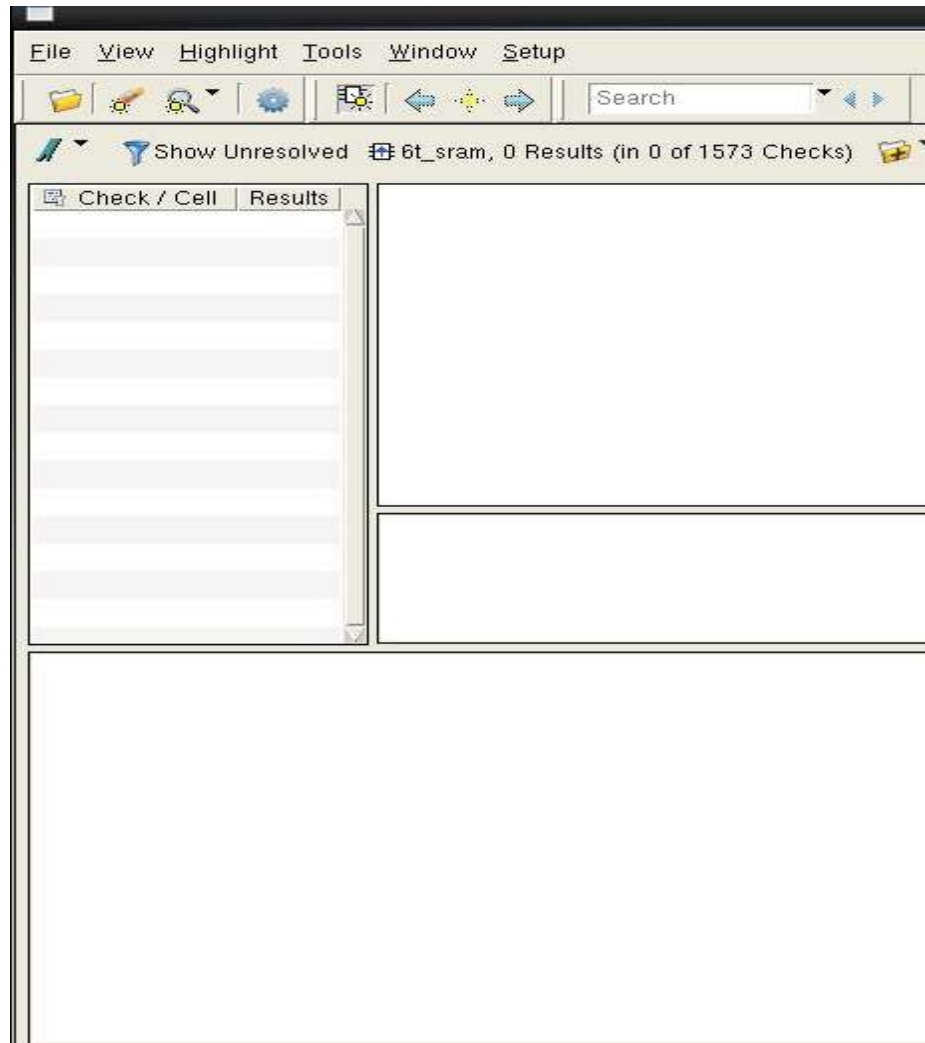

6T SRAM Array (4*4)

 


- **Cell Current:** SS Corner, taking BL,BLB,WL and VDD all equal to 1V, Temp=125C
- **Leakage Current:** TT Corner, taking BL,BLB,WL and VDD all equal to 1.1V and Temp =25C


FOMs-

- **Cell Current:** taking BL,BLB,WL,VDD,Q all equal to 1V and QB=0V then while doing DC Analysis, the current flowing through Pass Gate is Cell Current.
- **Leakage Current:** taking BL,BLB,WL, VDD and Q all equal to 1.1V and QB=0 then while doing DC Analysis, current flowing through VDD and BLB is Leakage Current.
- **Write Margin:** Taking WL=0, DC analysis and varying BL 0 to voltage at which Q and QB flips.
- **Write Time:** Time at which both 1s and 0s written inside the memory cell.
- **SNM:** Cross point of Q and QB in DC Analysis, keeping WL=0
- **6-Sigma:** Monte Carlo is run and see the HISTO graph.


Results – FOMs

 


Cell Current

 

Write margin

 



Leakage Current

 


Write Time

SNM, 6sigma qualification

(1/1)

  


SNM

 

PDF

HISTO

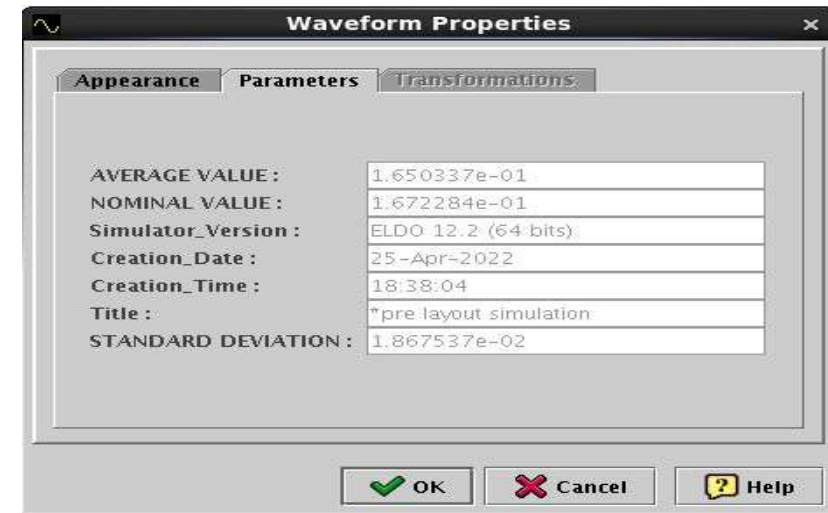

6 sigma qualified

Results



FOM	Value
Cell Current	53.06uA
Leakage Current	45.22pA
Write Margin	0.44volt
Write Time	77psec
SNM	0.54volt
Monte Carlo	6 sigma qualified

PVTs	Cell current
SS/25/1v	32.29uA
SS/125/1v	28.89uA
SS/-40/1v	35.95uA
TT/25/1v	41.89uA
TT/125/1v	37.2uA
TT/-40/1v	46.66uA
FF/25/1v	54.89uA
FF/125/1v	48.54uA
FF/-40/1v	61.03uA

Conclusions and Future Plans



◆ Technical Conclusions

- We were able to design a memory cell with the specified constraints and mirror it to obtain the memory cell.
 - It got difficult for us to convert into a 512x512 memory array.

◆ Learnings from the project

- We learnt to calculate different Figure of Merits and how to figure out the sizing using the Pull Up Ratio and Cell Ratio.
- We learnt what voltage of devices to use such that the design can be obtained for the given specification.
- The project helped us in better understanding of the theory portion taught in class by giving us a hands-on experience on the same for example the concept of mirroring.

◆ Future plans

- In SRAM Cell high Read current is needed so that it is sufficiently stable so in that process, while increasing the cell size, the leakage current also increases causing huge power overhead so ways can be looked at which does not lead to this.
- Memories having separate Read Write port can be explored
- Publication Scope in conferences like IOP Conference Series Materials Science and Engineering can be explored.

References



https://www.academia.edu/30689972/High_Read_Stability_and_Low_Leakage_Cache_Memory_Cell?email_work_card=view-paper

https://eecs.wsu.edu/~daehyun/teaching/2017_EE466/labs/EE586_CadTutorials_Ver2.pdf

https://www.academia.edu/17157991/Design_of_6T_5T_and_4T_SRAM_Cell_on_Various_Performance_Metrics?email_work_card=view-paper

https://www.academia.edu/7411497/Low_power_single_bitline_6T_SRAM_cell_with_high_read_stability?email_work_card=view-paper

<http://www.iosrjournals.org/iosr-jvlsi/papers/vol8-issue1/Version1/E0801014346.pdf>

https://www.academia.edu/30689972/High_Read_Stability_and_Low_Leakage_Cache_Memory_Cell?email_work_card=view-paper

https://www.academia.edu/13779655/DESIGN_OF_LOW_POWER_SRAM_CELL_WITH_IMPROVED_STABILITY?email_work_card=view-paper